


Experiment number -2

L3-B

group-12

Pre-Lab work :-



1.

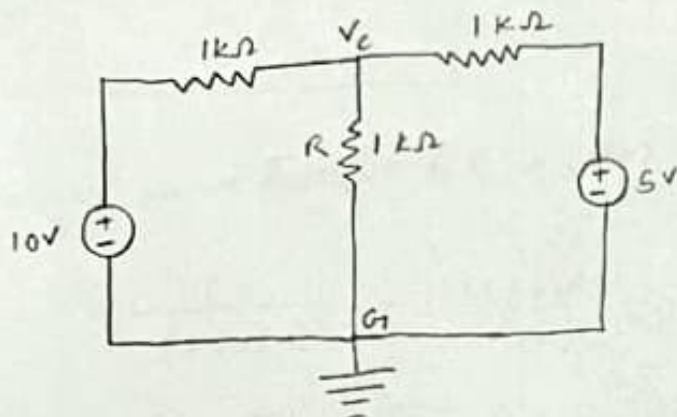

$$\frac{V_c - 10}{1k\Omega} + \frac{V_c - 5}{1k\Omega} = \frac{0 - V_c}{1k\Omega}$$

$$3V_c = 15$$
$$V_c = 5V \checkmark$$

2.

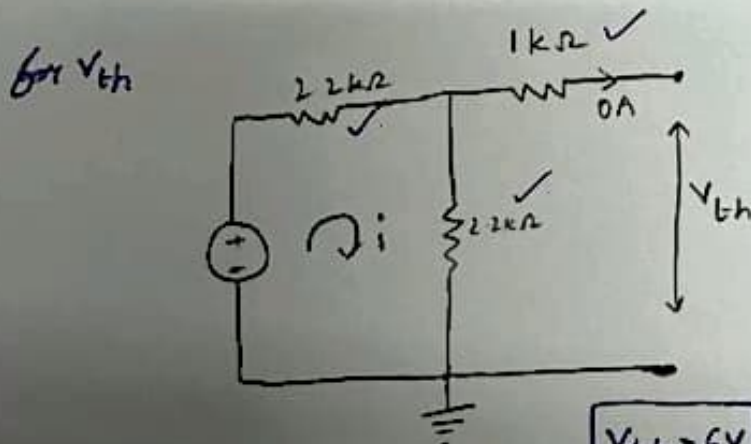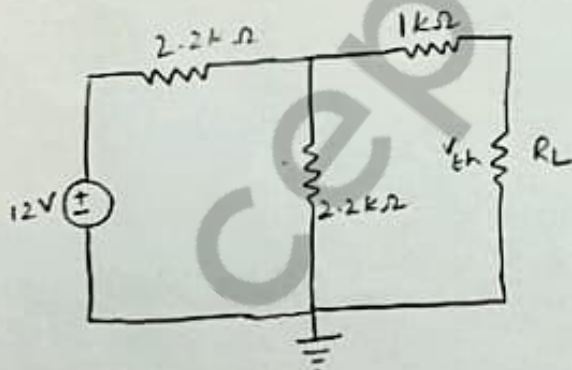


$$V_{th} = \frac{12 \times 2.2k}{(2.2k + 2.2k)} = 6V$$

$$R_{th} = 1k + \left(\frac{2.2 \times 2.2}{2.2 + 2.2} \right)k$$
$$= 2.1k\Omega$$

$V_{th} = 6V \checkmark$

$R_{th} = 2.1k\Omega \checkmark$

Equivalent circuit :-

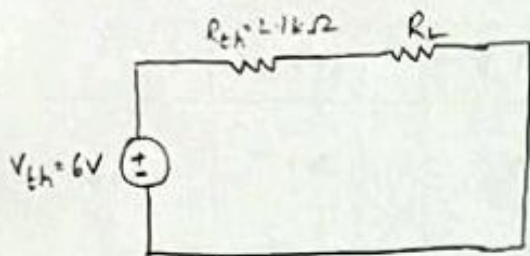

Maximum power transfer to R_L is when $R_L = R_{th}$

$$\Rightarrow i = \frac{6}{(2.1 + 2.1) k\Omega} = 1.428 \text{ mA}$$

$\therefore$ Power through R_L

$$P_L = i^2 R_L$$

$$= (1.428)^2 \times 2.1$$

$$P_L = 4.28 \text{ mW}$$

Mayank
4/4/22

PART-A: Superposition Theorem

	V_1 (V)	V_2 (V)	V_A (V)	V_O (V)	V_L (V)
Case-1	10	5	10	5	5
Case-2	10	0	10	0	3.3
Case-3	0	5	0	5	1.6

PART-B: Thevenin's Theorem

V_{OC} (V)	$V_{I_{sc}}$ (mV)	V_{Th} (V)	R_{Th} (k Ω)
6	28	6	2.14

PART-C: Maximum Power Transfer Theorem

R_L (Ω)	V_A (V)	V_L (mV)	I_L (mA)	Power (mW)
560	1.3	22	2.2	2.81
1000	1.9	19	1.9	3.57
2200	3.2	14	1.4	4.46
3900	3.9	10	1.0	3.89
4700	4.0	9	0.9	3.59

Wajant
4/4/22

Part-0 :-

1) (a) When $V_1 = 10V$, $V_2 = 5V$
we get, $V_{C_1} = 5V \dots (i)$

(b) When $V_1 = 10V$, $V_2 = 0V$
we get, $V_{C_2} = 3.3V \dots (ii)$

(c) When $V_1 = 0V$, $V_2 = 5V$
we get, $V_{C_3} = 1.6V \dots (iii)$

Thus from (ii), (iii) we get

$$V_{C_2} + V_{C_3} = 4.9V$$

$$\text{So, we have \% error} = \frac{5 - 4.9}{5} \times 100 \checkmark$$
$$= 2\% \checkmark$$

$$\text{Hence, we have \% accuracy} = 98\%$$

Sources of error :-

- (i) Error may occur due to loose connections. ✓
- (ii) Error may occur due to parallax in oscilloscope reading.
- (iii) There may be instrumental error. ✓


$$2) (V_{Th})_{Theoretical} = 6V$$

$$(V_{Th})_{expt} = 6V$$

$$(R_{Th})_{Theoretical} = 2100 \Omega$$


$$(R_{Th})_{expt} = 2142 \Omega$$

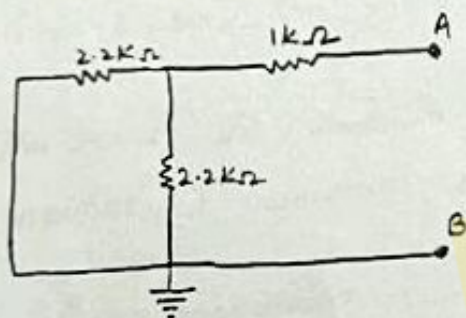Calculation of R_{Th} (Theoretical) :- circuit diagram



$$R_{AB} = R_{Th} (Theoretical)$$

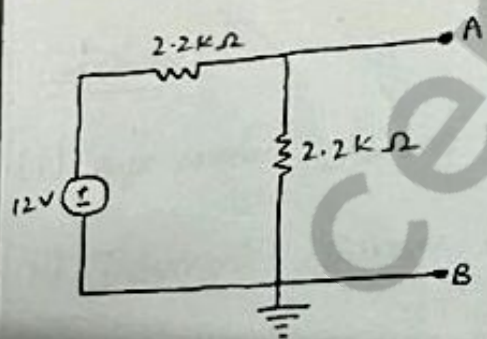Calculation of V_{Th} (Theoretical) :- circuit diagram.



$$V_{AB} = V_{Th} (Theoretical)$$

→ No difference in V_{Th} values

→ Difference in R_{Th} values

$$\% \text{ error} = \frac{2100 - 2142}{2100} \times 100 = -2\%$$

✓
18/4/22.

Source of error :-

- (i) Loose connection
- (ii) Parallax error in oscilloscope reading.
- (iii) resistance in connecting wires.
- (iv) other instrumental error.

3) Maximum power in part(c) is when R_L is nearer to R_{Th}
i.e. 2200Ω

This proves the maximum power transfer theorem that power consumed is maximum when $R_L = R_{Th}$

Power maximum :- $R_L = 2200\Omega$

$$P_{max} = 4.2 \times 10^{-3} W$$

Conclusion :-

- (i) Superposition Theorem is verified ; (Port A)
- (ii) Thevenin's Theorem is verified ; (Port B)
- (iii) Maximum Power Transfer Theorem is verified ; (Port C)

P_{max} across R_L is when

$$R_L = R_{Th}$$

Experiment number-3

L3-B

Group-12

Pre-Lab work:-

1)

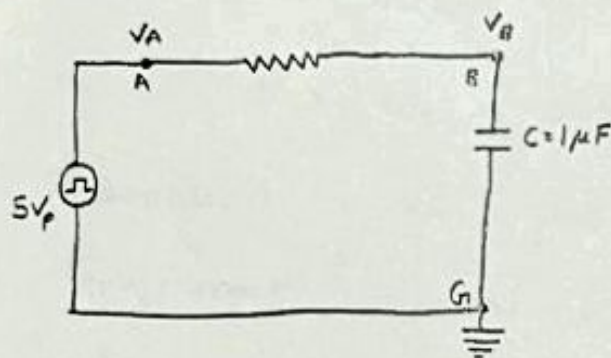


Fig. 1

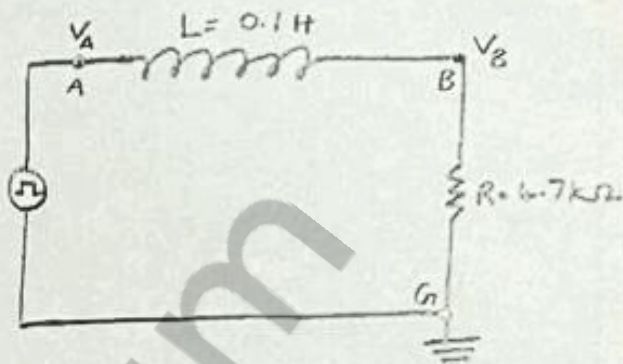


Fig. 2

Sol:-

For Fig. 1 $\rightarrow$ RC circuit

$$\text{Time constant} = \tau_1 = RC$$

$$= (1 \times 10^3)(1 \times 10^{-6}) \text{ sec}$$

$$= 10^{-3} \text{ sec}$$

$$= 1 \text{ msec} \checkmark$$

For Fig. 2 $\rightarrow$ LR circuit

$$\text{Time constant} = \tau_2 = \frac{L}{R}$$

$$= \frac{0.1 \text{ H}}{4.7 \times 10^3 \Omega}$$

$$= \frac{10^{-3}}{47} \text{ sec}$$

$$= 2.13 \times 10^{-5} \text{ sec}$$

$$= 0.0213 \text{ ms} \checkmark$$

2)

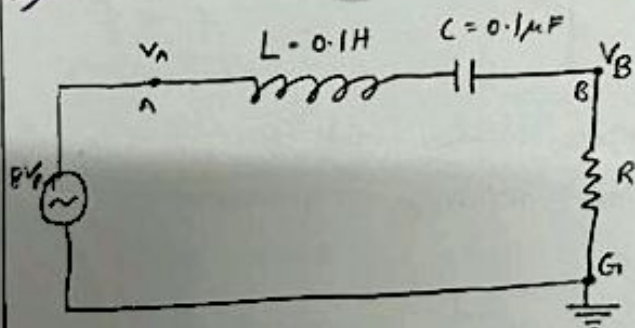


Fig-3

$$\text{Sol:- Impedance} = Z = R + j \left(\omega L - \frac{1}{\omega C} \right)$$

$$\text{Resonant frequency} \Rightarrow \text{Im}(Z) = 0$$

$$\omega L - \frac{1}{\omega C} = 0$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega = \frac{1}{\sqrt{(0.1 \text{ H})(0.1 \times 10^{-6} \text{ F})}}$$

$$= 10^4 \text{ rad/s}$$

$$\omega = 2\pi f$$

$$f = 1591.55 \text{ Hz}$$


$$\omega = 10^4 \text{ rad/sec}$$

Ans

PART - A :

STEP RESPONSE OF RC CIRCUIT

1.

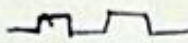$V_{\text{peak}} = 5\text{V}$ square wave 

frequency = $0.1\text{kHz} = 100\text{Hz}$

$V_x = 5 \times 0.63 = 3.15\text{VOLT}$


$\tau_{\text{theoretical}} = RC = 1000 \times 10^{-6} = 10^{-3}\text{s} \checkmark$

$\tau_{\text{experimental}} = 1\text{ms} \checkmark$

$T = \frac{1}{f} = \frac{1}{100} = 10\text{ms}$

$\frac{T}{\tau} = \frac{10\text{ms}}{1\text{ms}} = 10 \checkmark$

2.

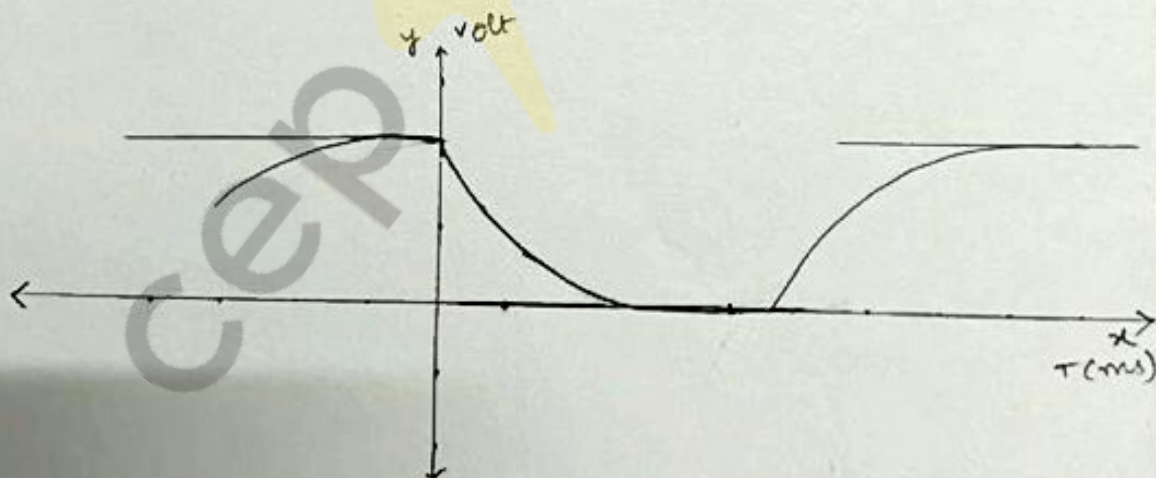

3. Frequency for which capacitor just gets charged upto maximum possible voltage = 100Hz


$\tau = 1\text{ms}$

$T = \frac{1}{f} = \frac{1}{100\text{Hz}} = 10\text{ms} \checkmark$

$\frac{T}{\tau} = \frac{10\text{ms}}{1\text{ms}} = 10 \checkmark$

Signature
18/4/22.

PART-B: STEP RESPONSE OF RL CIRCUIT

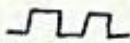
1. $V_{\text{peak}} = 5V$ square wave 

frequency = $499.3 \text{ Hz} \approx 0.5 \text{ kHz}$

$$V_z = 4.98 \times 0.63 \approx 3.14 \text{ V}$$

$$\tau_{\text{theoretical}} = \frac{L}{R} = \frac{0.1 \text{ H}}{4.7 \times 10^3} = 2.13 \times 10^{-5} \text{ sec} \approx 21 \mu\text{sec}$$
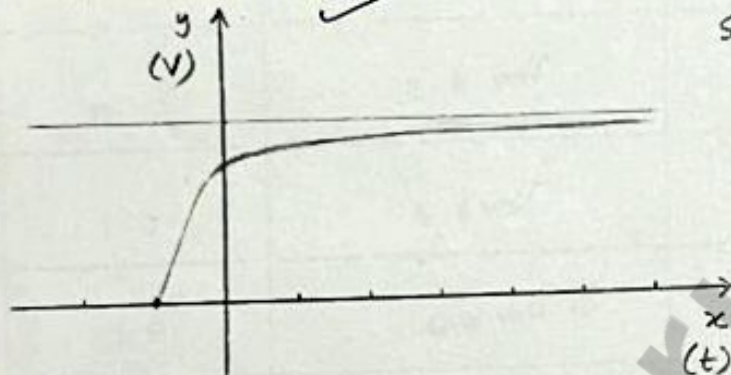
$$\tau_{\text{experimental}} = 20 \mu\text{sec} \quad \checkmark$$



SCALE: X-axis $\rightarrow 1 \text{ cm} = 20 \mu\text{s}$

Y-axis $\rightarrow 1 \text{ cm} = 2 \text{ V}$

$$T = \frac{1}{f} = \frac{1}{499.3} \approx 2 \text{ m sec.} \quad \checkmark$$

Signature
18/4/22

Part C:- Resonance in series RLC circuit:-

182:-

Frequency (kHz)	voltage across terminal (B-G) (volt)	current in RLC $I = V_{BG}/R = 1K$
0.1	0.54 volt	0.54 mA
0.5	2.4 volt	2.4 mA
1.0	4.6 volt	4.6 mA
1.5	5.5 volt ✓	5.5 mA
2.0	5.2 volt	5.2 mA
4.0	3.1 volt	3.1 mA
10.0	1.3 volt	1.3 mA

3. Coarse estimate of the resonant frequency = 1.5 kHz

V_{BG} at resonance = 5.5 volt
(Coarse) ✓

5. Phase difference at $f = 0.1$ kHz
nature $\Rightarrow$ lagging leading

$$\text{Phase difference} = \frac{2.2 \times 10^{-3} \times 360}{10^{-4} \times 100} = 79.2^\circ \text{ (lag)}$$

6 ~~f = 10~~

Phase difference at $f = 10 \text{ kHz}$.

nature $\Rightarrow$ leading

$$\text{Phase difference} = \frac{22 \times 10^{-6} \times 360}{0.1 \times 10^{-3}} = 79.2^\circ \quad \begin{matrix} \text{(lead)} \\ \text{Lagging} \end{matrix}$$

Page No.
 18/4/22.

Part D:-

$$1) \omega_{\text{theoretical}} = \frac{1}{\sqrt{LC}} = 10 \text{ krad/s}$$

$$f_{\text{theoretical}} = \frac{1}{2\pi\sqrt{LC}} = 1591.55 \text{ Hz} \checkmark$$

$$\omega_{\text{experimental}} = 2\pi f_{\text{experimental}}$$

$$f_{\text{experimental}} = 1550 \text{ Hz} \checkmark$$

$$\omega_{\text{experimental}} = 9.73 \text{ krad/s}$$

Error in estimated resonant frequency can occur due to

- (i) resistance in connecting wires
- (ii) Resistance in instruments used.
- (iii) change in resistances due to heating
- (iv) loose connections

$$2) (a) \text{ for } \omega = 0.1 \text{ kHz}$$

$$\omega < \omega_R$$

$$\text{so, } \omega L < \frac{1}{\omega C} \rightarrow X_L < X_C$$

$$X_C - X_L > 0 \rightarrow \text{circuit is capacitive} \checkmark$$

so current leads voltage in circuit or voltage lags current in circuit

$$(b) \text{ for } \omega = 10 \text{ kHz}$$

$$\omega > \omega_R$$

$$\text{so } \omega L > \frac{1}{\omega C} \rightarrow X_L > X_C$$

$$X_L - X_C > 0 \rightarrow \text{circuit is inductive} \checkmark$$

so current lags voltage or voltage leads current in circuit.

$$3) \text{ At } \omega = \frac{1}{\sqrt{LC}} = 10^4 \text{ rad/s or } f = 1.59 \text{ kHz}$$


Phase difference $\phi = 0$, Net (Impedance) $= Z = R$ ($X_L = X_C$)

$$V_R = V = V_0 \sin \omega t$$

$$i = \frac{V_0}{R} \sin \omega t = i_R$$

$$V_C = \frac{q}{C} = \frac{V_0}{RC} \sin \omega t \\ = V_0 \sin(\omega t - \pi/2)$$
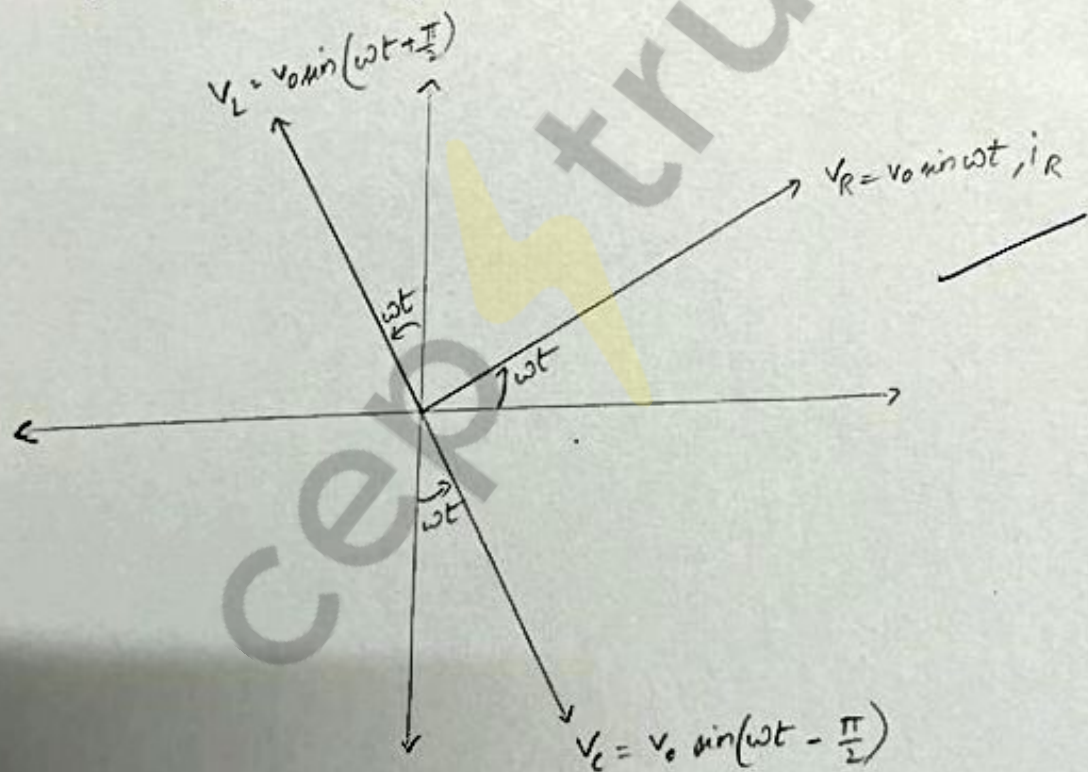
$$V_L = L \frac{di}{dt} = \frac{V_0 \omega L}{R} \sin(\omega t + \frac{\pi}{2}) = V_0 \sin(\omega t + \pi/2)$$




Experiment-4

AL3-B
Group-12

Pre-Lab

Ans 1.

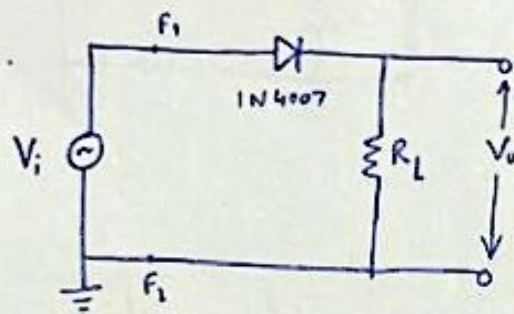


$$V_i = 10 \text{ V (pp)}$$

$$f = 500 \text{ Hz}$$


$$R_L = 2.2 \text{ k}\Omega$$

$$V_D = 0.7 \text{ V}$$

$$V_o (\text{expected}) = 8.6 \text{ V (pp)}$$

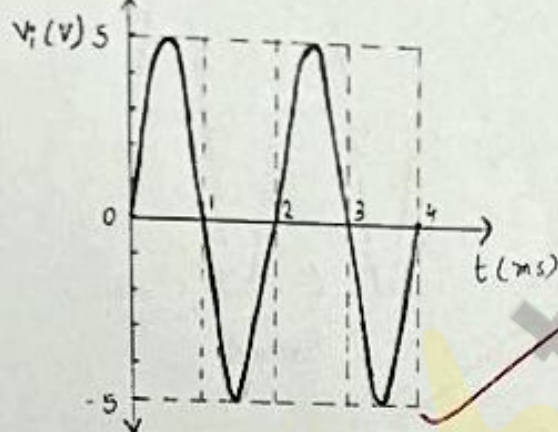


channel 1

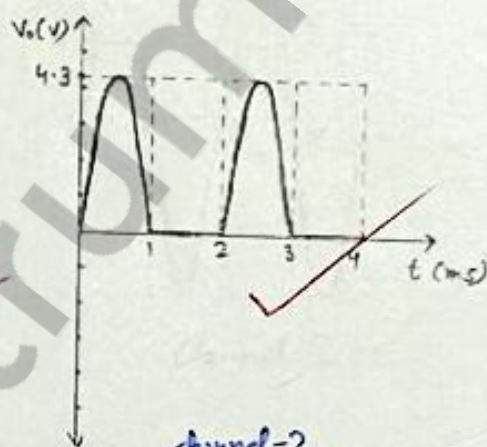

channel-2

Ans 2.

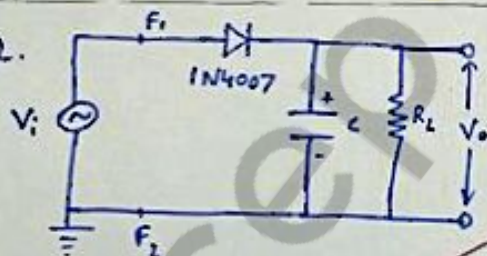


$$V_i = 10 \text{ V (pp)}$$

$$f = 500 \text{ Hz} \Rightarrow T = 2 \text{ ms}$$


$$R_L = 2.2 \text{ k}\Omega, C = 22 \mu\text{F}$$

$$V_{dc} = \left(1 - \frac{T}{2R_L C}\right) S = 4.896 \text{ V}$$

$$(V_i)_{rr} = \frac{T}{R_L C} \times 5 = 0.208 \text{ V}$$

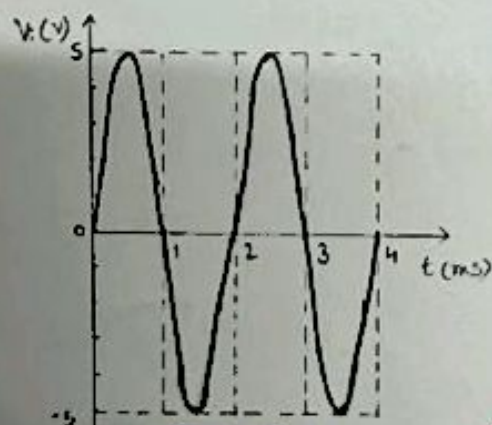


Channel 1

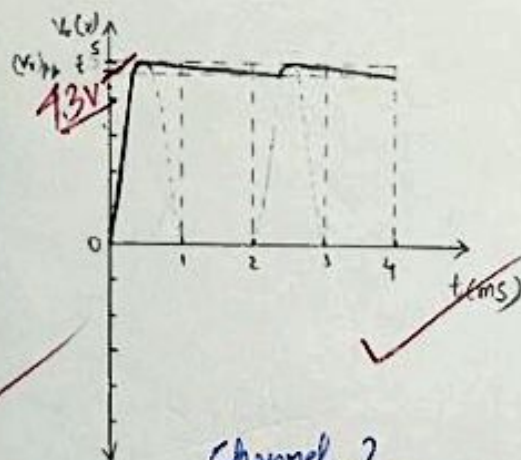


Channel 2


Ans 3.

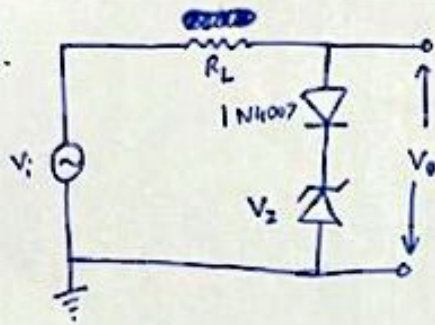

$$\begin{aligned} V_i &= 20\text{V (rms)} \\ f &= 500\text{Hz} \\ V_2 &= 3.9\text{V} \\ R &= 2.2\text{k}\Omega \\ V_d &= 0.7\text{V} \end{aligned}$$

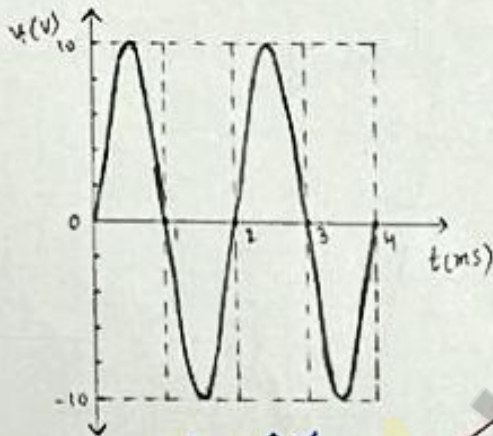

channel 1

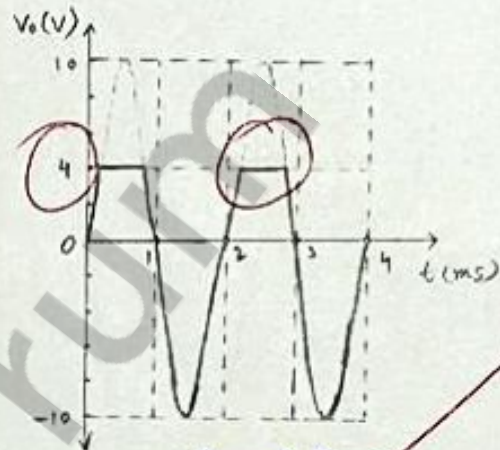

channel 2

Rahul
25/01/22


$V_1 (V)$

CHANNEL-1

SCALE: (For both channels)

X-axis $\rightarrow$ 1 unit = $\frac{1}{3}$ sec.

Y-axis $\rightarrow$ 1 unit = 1 Volt

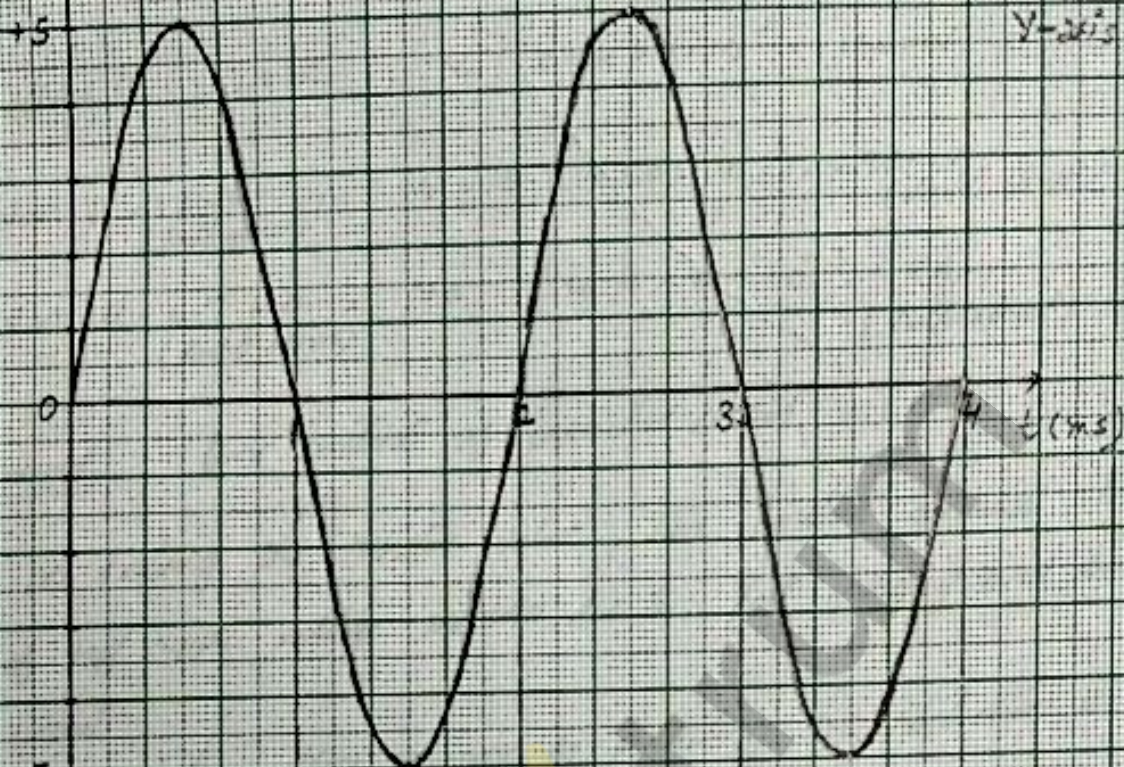

$V_0 (V)$

CHANNEL-2

+5
+4V




Answers
2/11/22

CHANNEL-1


SCALE: (For both channels)

X-axis $\rightarrow$ 1 grid = 0.5 ms

Y-axis $\rightarrow$ 1 grid = 1 Volt

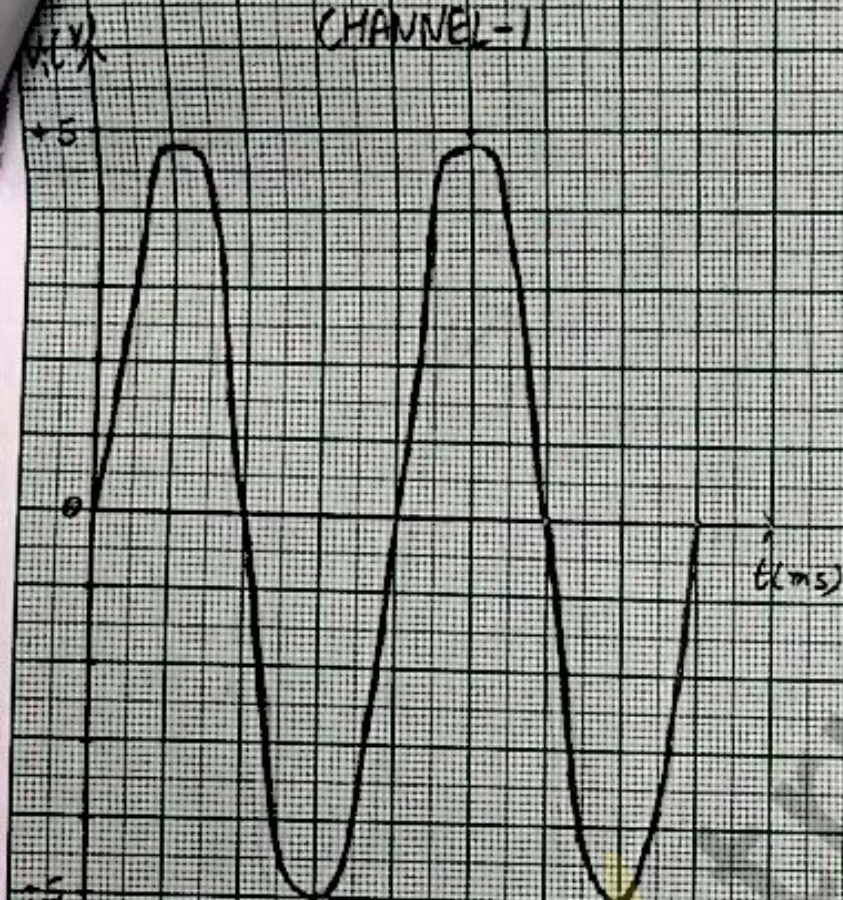


CHANNEL-2

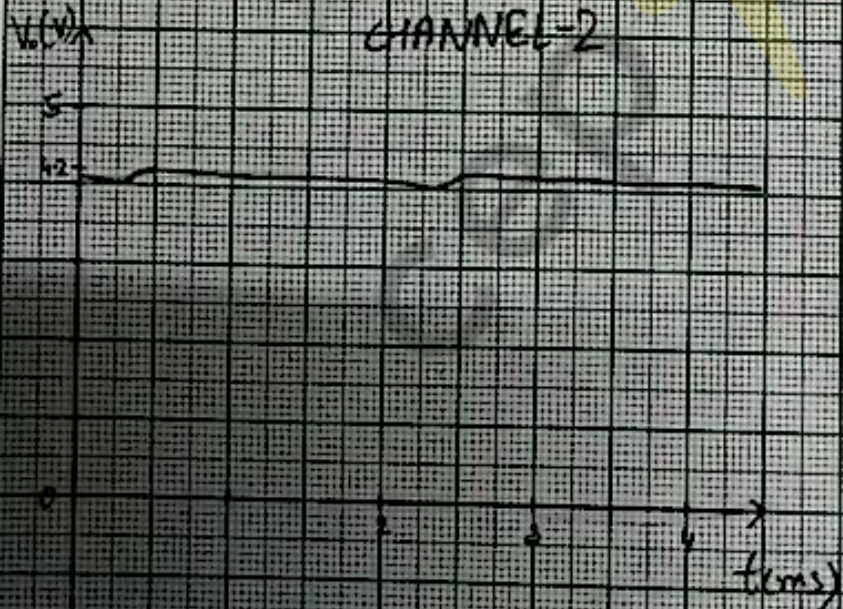

Signature
25/4/22


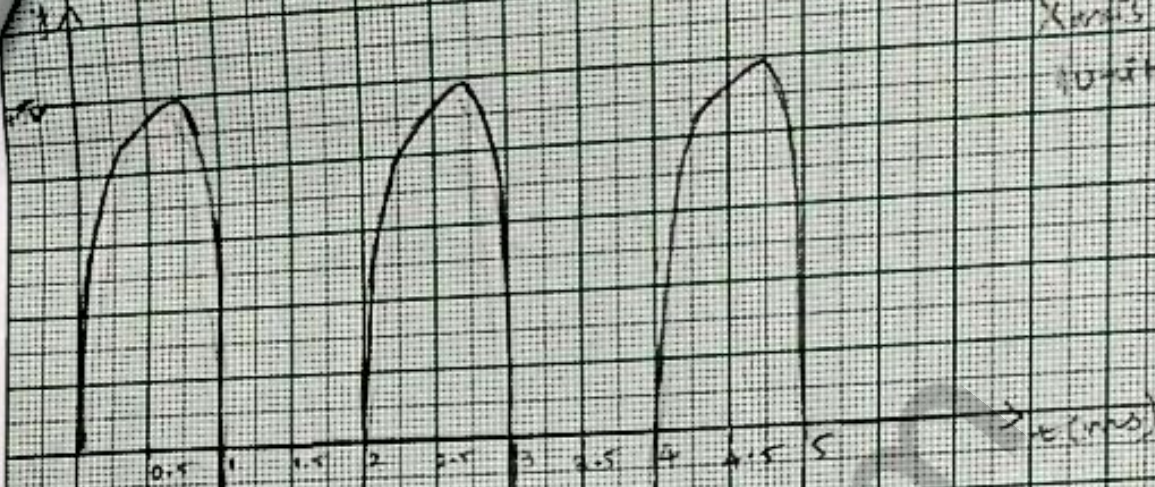
Y-axis: Input voltage
 Unit = V
 X-axis: time axis
 Unit = 0.5 ms



Y-axis: output voltage
 Unit = V
 X-axis: time axis
 Unit = 0.5 ms



✓
 05/4/22

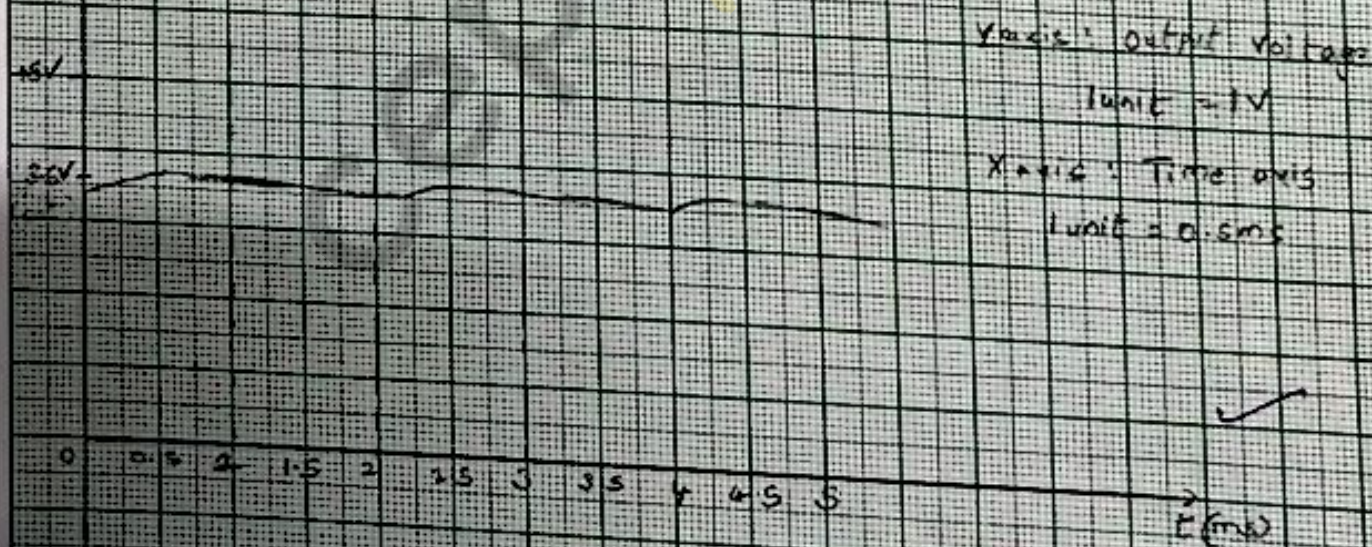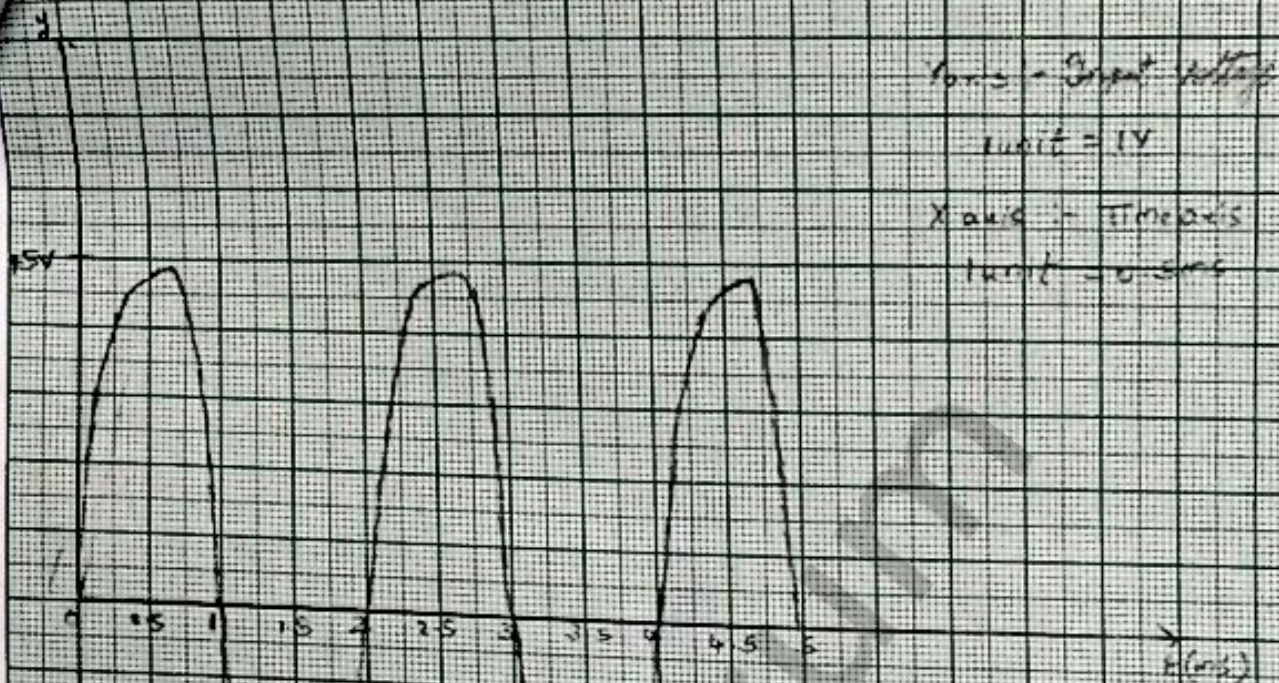

✓

Output
2.5 V/Div

Part-B:-

$$V_{\text{input}} = 10 \text{ volt}$$

$$\text{when } R = 2.2 \text{ k}\Omega, \quad V_0 = 3.1 \times 50 \times 10^{-3} = 155 \text{ mV}$$

$$\text{when } R = 1 \text{ k}\Omega \quad (half \text{ approx}), \quad V_0 = 5.8 \times 50 \times 10^{-3} = 290 \text{ mV} \quad (\text{double almost})$$

$$\text{when } R = 4.7 \text{ k}\Omega \quad (\text{double approx}), \quad V_0 = 4.4 \times 20 \times 10^{-3} = 88 \text{ mV} \quad (\text{half almost})$$

Comment :- time constant of capacitive circuit = RC

→ on halving the resistor value, time constant decreases, thus amplitude of ~~high~~ ripple voltage increases due to fast charging and discharging of circuit.

Here ripple voltage is more so pulsating DC fluctuation is more.

→ on doubling the resistor value, time constant increases, thus amplitude of ripple voltage ~~is~~ decreases due to slow charging and discharging of circuit.


Here ripple voltage is less so pulsating DC fluctuation is less.

50

Scale

x-axis unit = 0.001s

y-axis unit = 1V

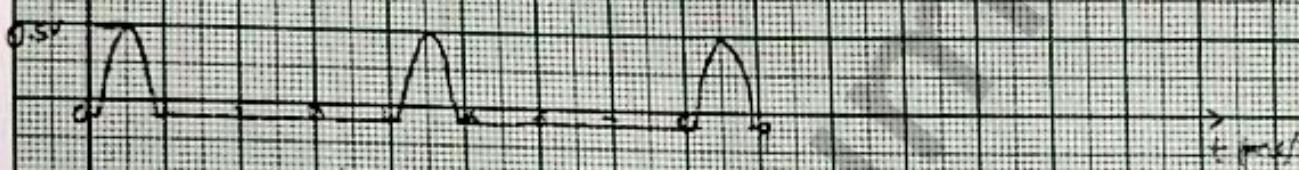


Scale

x-axis =

unit = 0.001s

y-axis =

unit = 1V

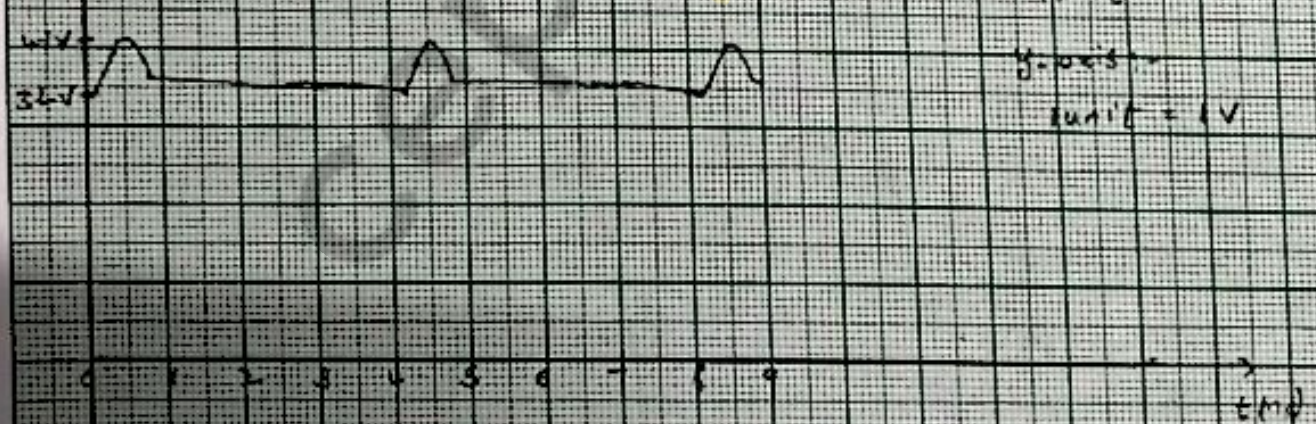

✓

Chapman

8/5/22


$V_1(t)$

CHANNEL-1

SCALE:


$X = 2 \mu s \rightarrow 1 \text{ unit} = 0.5 \text{ ms}$

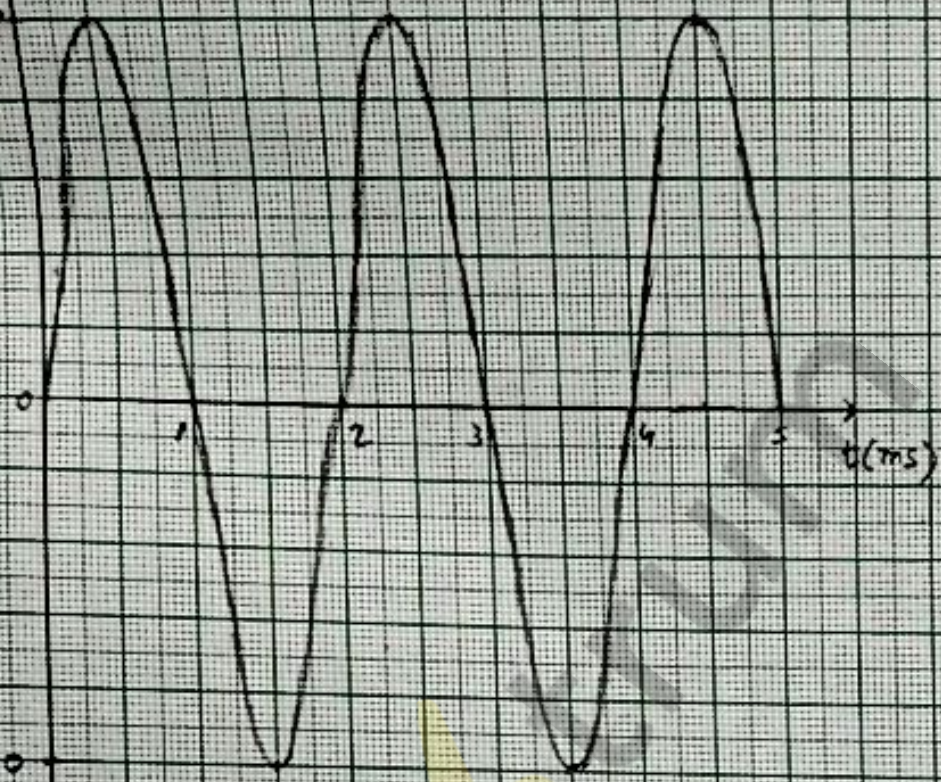$Y = 2 \text{ V} \rightarrow 1 \text{ unit} = 1 \text{ V}$




$V_2(t)$

CHANNEL-2

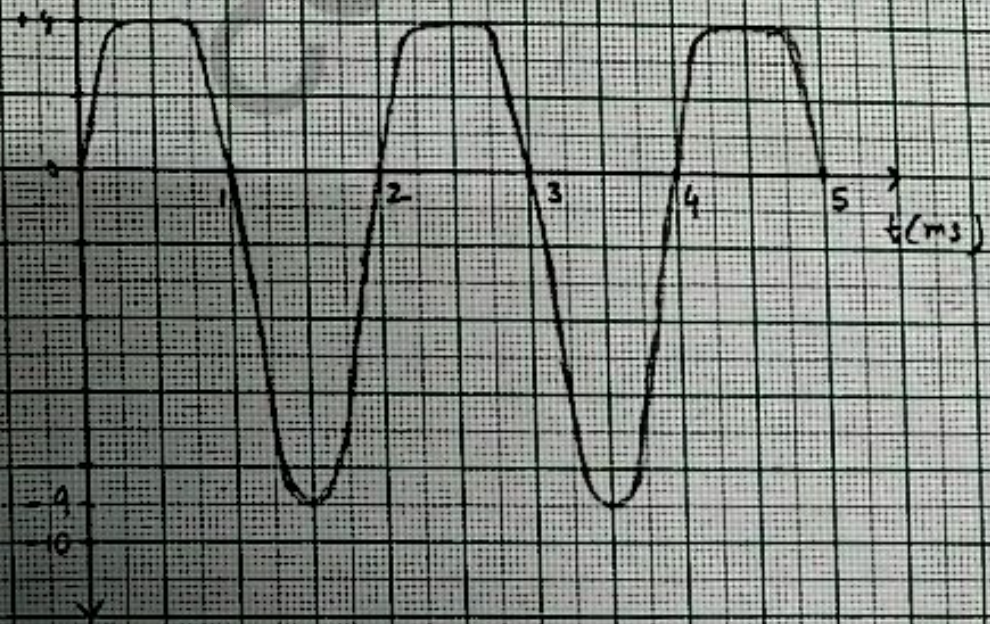

Signature
25/4/22

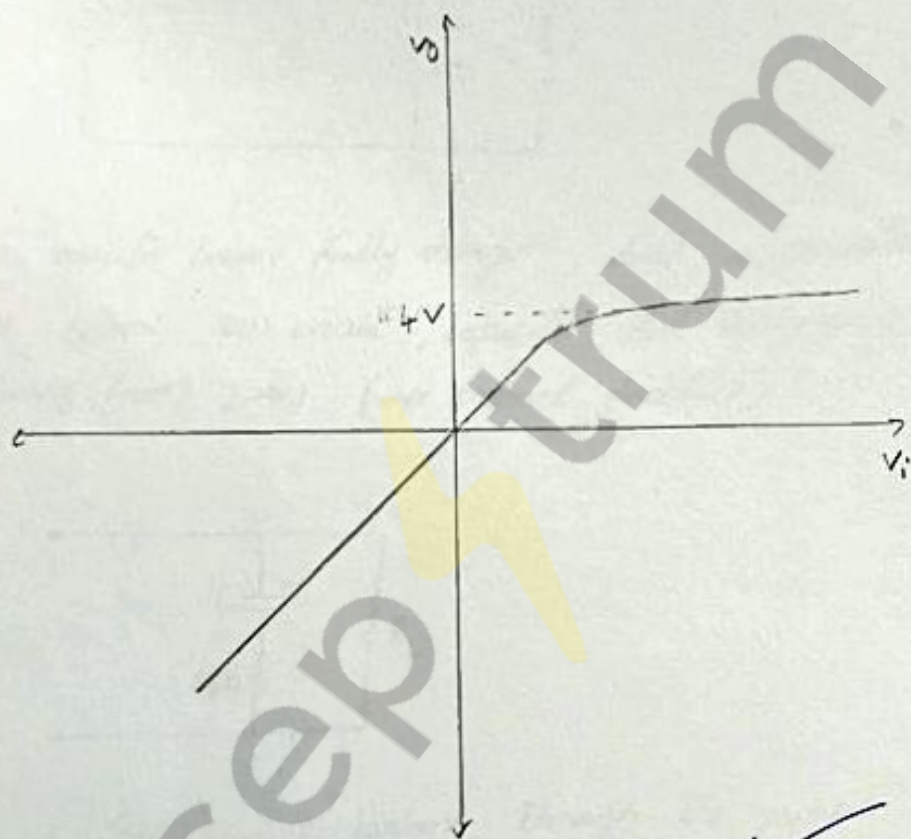


✓


Dayan
25/4/22.

nt. P:-

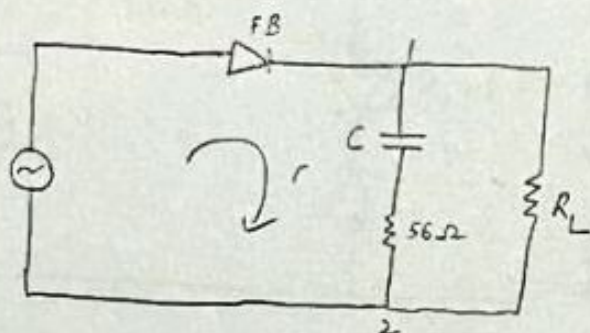- ① when capacitor is charging, diode is in forward bias, current is flowing from 1 $\rightarrow$ 2 (+ve current direction)




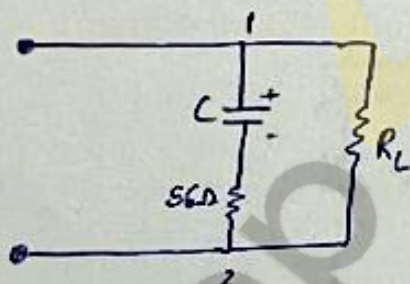- ② when capacitor become fully charged, diode is in reverse bias, voltage source become open circuit, capacitor start discharging, so current is flowing from 2 $\rightarrow$ 1 (-ve current direction)



so $I_C (-V_{56}/56)$ $\rightarrow$ the current through the capacitor, negative for some portion of cycle as shown in part ②.

Estimation of $(I_C)_{\text{peak}}$:-

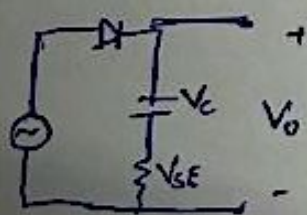

$$V_0 = V_C + V_{56} = i_C \times Z$$

$$i_C = \frac{V_0}{Z}, i_{C, \text{max}} = \frac{V_{0, \text{max}}}{Z}, V_{0, \text{max}} = (V_i)_{\text{max}} - 0.7$$

$$(V_0)_{\text{max}} = 5 - 0.7 = 4.3 \text{ V}$$

$$(V_0)_{\text{max}} = 4.3 \text{ V} \quad Z = \sqrt{X_L^2 + R^2}, \quad X_L = \frac{1}{j\omega C}, \quad \omega = 2\pi \times 500 \times 10^3 \text{ rad/s}$$

$$(i_C)_{\text{max}} = \frac{4.3}{Z} = 0.0743 \text{ A}$$

$$Z = 57.84 \Omega$$


$$X_L = 14.46 \Omega$$

$$C = 22 \times 10^{-6} \text{ F}$$


$$R = 56 \Omega$$

$$(i_C)_{\text{max}} = 0.0743 \text{ A}$$

-ve clipper

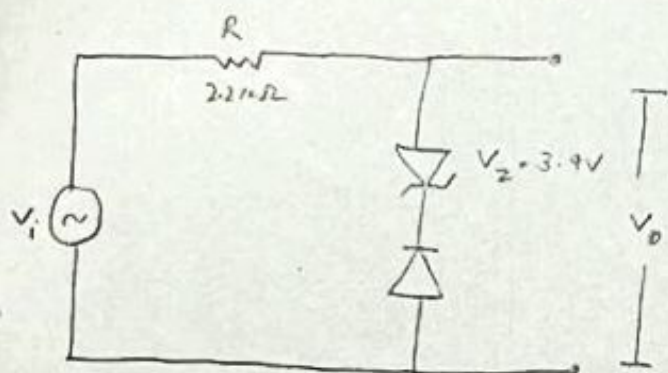

(b) +ve & -ve clipper

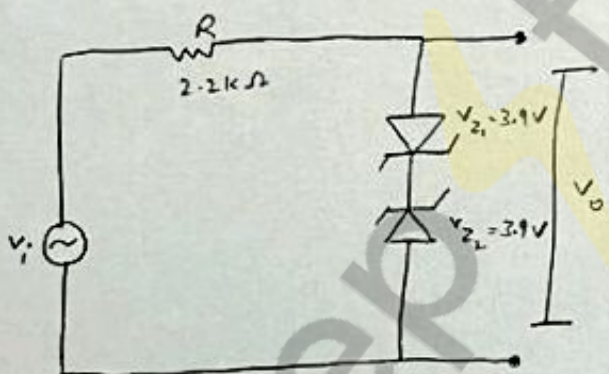


✓
14/5/22


PART-A: Unregulated Power Supply - Full Wave Rectifier (FWR)

1. Transformer $T_x \rightarrow 230V$ to $12-0-12V$, $1A$ and $R_L = 1k\Omega$ rating

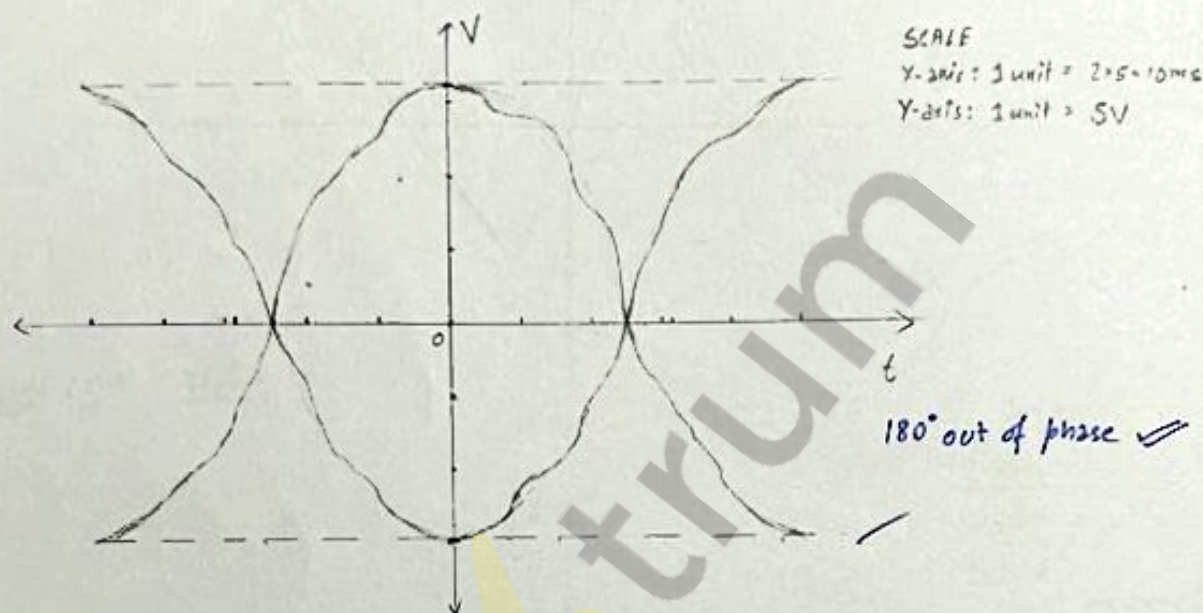2. $V_{ab} = 3 \times 5 = 15V$ multiplier = 5
 $V_{bg} = 3.2 \times 5 = 16V$ time scale = 2ms



3.

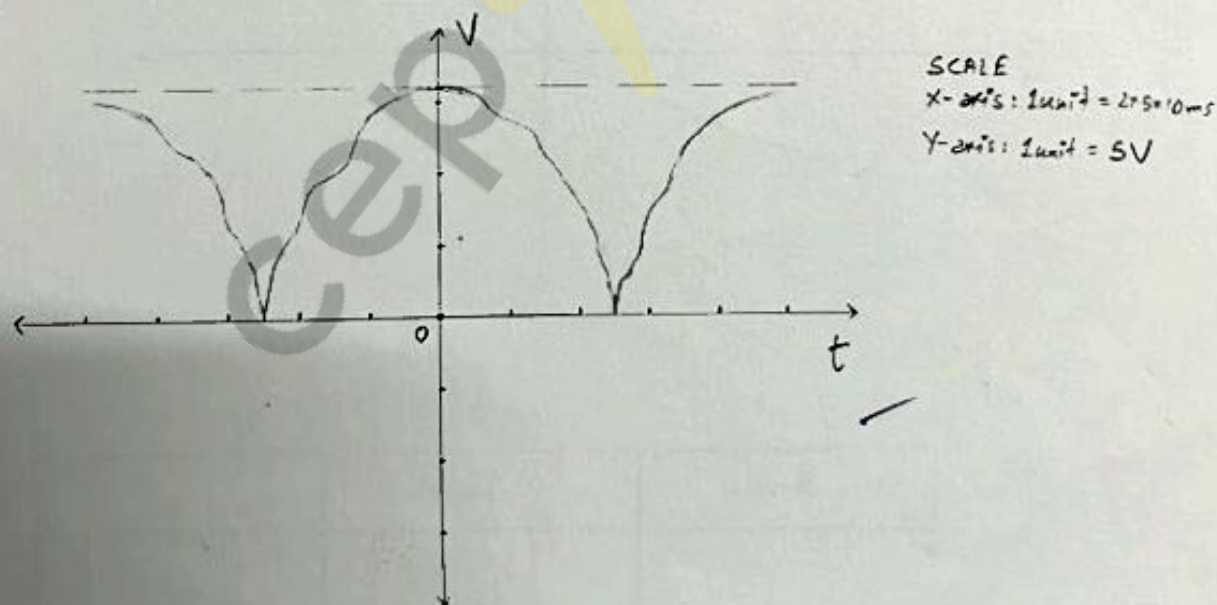

full wave rectifier :-


Scale :-

y-axis :-

1 unit $\rightarrow$ 0.5V/div

x-axis :-

1 unit $\rightarrow$ 2ms/div

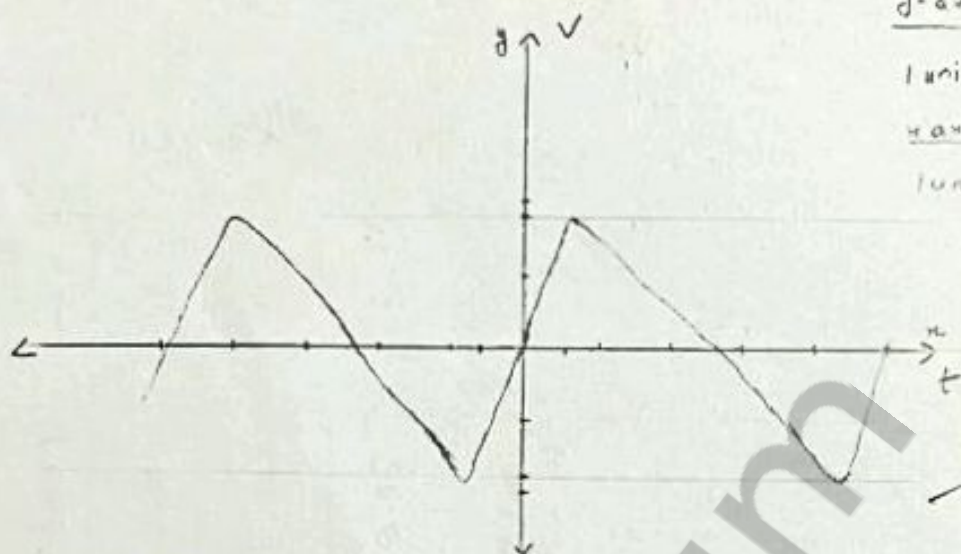

Half wave rectifier :-


Scale :-

y-axis :-

1 unit $\rightarrow$ 1V/div

x-axis :-

1 unit $\rightarrow$ 2ms/div

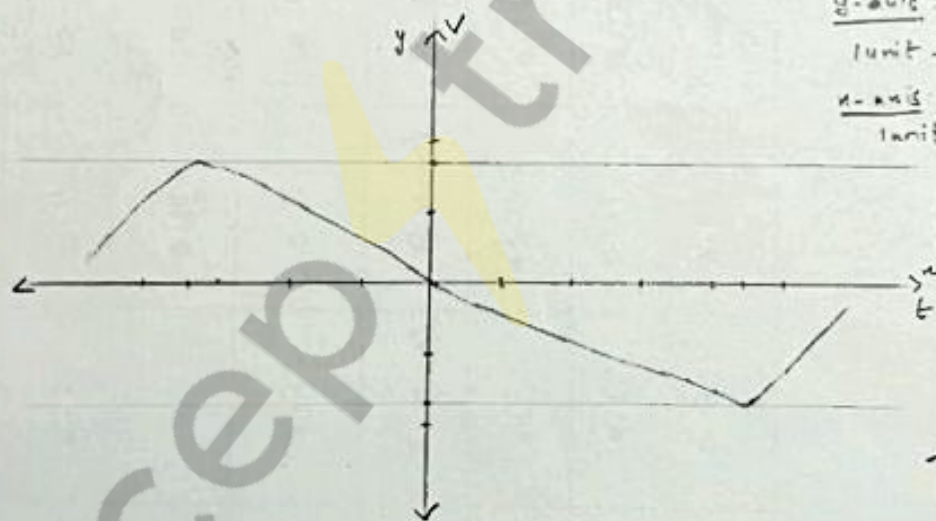

	FWR	H.W.R
V_r	1.7V ✓	3.2V ✓

PART - B : Regulated power supply - Zener regulator

R_L	$V_o(\text{max})$	$V_r(\text{V})$	$V_{or}(\text{max})$	$V_{ir}(\text{V})$	$V_o(\text{avg})$	$V_{or}(\text{avg})$
∞	15.5	1.8	6.2	0.11	14.6	6.145
1K Ω	15.5	1.8	6	0.104	14.6	5.948
220 Ω	15.5	2	4.2	0.5	14.5	3.95
R_L	$I_R(\text{A})$	$I_L(\text{mA})$	$I_Z(\text{mA})$	$P_Z(\text{mW})$	$P_R(\text{W})$	% Reg
∞	0.0150	0	15	92.175	0.127	0
1K Ω	0.0155	5.9	9.6	57.1	0.134	3.2
220 Ω	0.0188	17.9	0.9	3.55	0.198	35.72

Signature
12/5/22

Part C :-

1. No, we didn't get the peak voltage in both the halves equal in step 3 of part A.

$$V_{AG1} = 15V$$

$$V_{BG1} = 16V$$

It is because centre tap is not proper

$$\text{Ripple Frequency in F.W.R} = \frac{1}{3.8 \times 5 \times 10^{-3}} \\ = 52.63 \text{ Hz}$$

$$\text{Ripple Frequency in H.W.R} = \frac{1}{5 \times 2 \times 10^{-3}} \\ = 100 \text{ Hz}$$

2. Yes, I_L have poor regulation it may be due to very small value of R_L . For $R_L = 220 \Omega$, percentage regulation is very high. Thus the poor regulation occurs due to very low value of R_L .

3. Given: $I_Z(\text{min}) = 5 \text{ mA}$
 $P(\text{max}) = 0.5 \text{ watt}$

$$V_{\text{max}} (\text{across zener}) = \frac{P_{\text{max}}}{I_{\text{min}}} = \frac{0.5}{5 \times 10^{-3}} = 100V$$

$$I_R = \frac{V_0 - V_Z}{R} = \frac{13.5 - 6}{960} = 13.9 \text{ mA}$$

we can modify the circuit by providing the higher value of R_Z for an even higher I_L . $R \times R_L$ are to be formula reduced greatly.

$$P_z = \frac{1}{2} W, \quad V_z I_z = \frac{1}{2} W$$

$$I_z = 83.3 \text{ mA}$$

$$I_R = I_z(\text{max})$$

$$R = \frac{V_0 - V_z}{I} = \frac{13.5 - 6}{83.3} = 108.04 \Omega$$

$$I_R = I_z(\text{min}) + I_z(\text{max}) = 83.3 - 5 = 78.3 \text{ mA}$$

$$4. \quad P = \frac{V^2}{R} = \frac{(7.5)^2}{108.4} = 520.6 \text{ mW}$$

Yes, we use our correct voltage resistance as due to maximum power assumed by resistance was less than power voltage

Byju's
21/5/22

Pre-Lab - 6

Group: 12

Ans 1. considering ideal op-amp,

$$V_+ = V_- = 0$$

from fig, $V_x = \frac{V_i}{2}$

Applying KVL $\rightarrow$

$$\frac{V_o - V_+}{R_1} = \frac{V_- - V_x}{R_2}$$

$$\Rightarrow \frac{V_o}{R_1} = -\frac{V_i}{2R_2}$$



$$\Rightarrow \boxed{\frac{V_o}{V_i} = -\frac{R_1}{2R_2}}$$

(i) $R_1 = 100\text{ k}\Omega$ & $R_2 = 10\text{ k}\Omega$

$$\therefore \frac{V_o}{V_i} = \frac{-100}{2 \times 10} = -5$$

(ii) $R_1 = 10\text{ k}\Omega$ & $R_2 = 1\text{ k}\Omega$

$$\therefore \frac{V_o}{V_i} = \frac{-10}{2 \times 1} = -5$$

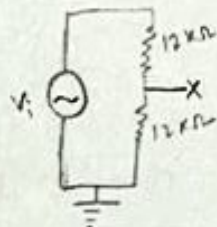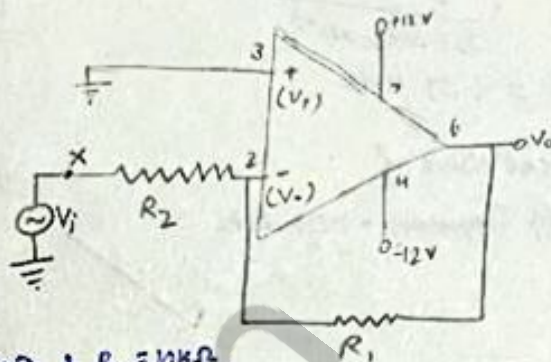

Ans 2. considering ideal op-amp

$$V_+ = V_- = V_x = \frac{V_i}{2} \text{ (From fig.)}$$

Applying KVL $\rightarrow$

$$\frac{V_o - V_-}{R_1} = \frac{V_- - 0}{R_2}$$

$$\Rightarrow \frac{V_o - V_i/2}{R_1} = \frac{V_i/2}{R_2}$$

$$\Rightarrow R_2 V_o = \frac{(R_1 + R_2)}{2} V_i$$


$$\Rightarrow \boxed{\frac{V_o}{V_i} = \frac{R_1 + R_2}{2R_2}}$$

(i) $R_1 = 100\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$

$$\therefore \frac{V_o}{V_i} = \frac{110}{2 \times 10} = 5.5$$

(ii) $R_1 = 10\text{ k}\Omega$, $R_2 = 1\text{ k}\Omega$


$$\therefore \frac{V_o}{V_i} = \frac{11}{2 \times 1} = 5.5$$

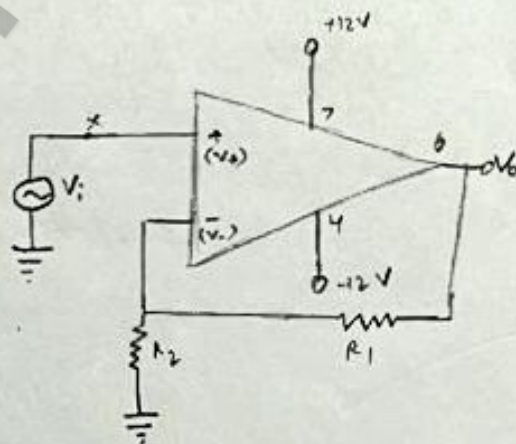

Ans 2. cut-off frequency

$$\begin{aligned} f_c &= \frac{1}{2\pi RC} \\ &= \frac{1}{2\pi \times 1000 \times 10^{-7}} \\ &= 1.59 \text{ kHz} \end{aligned}$$

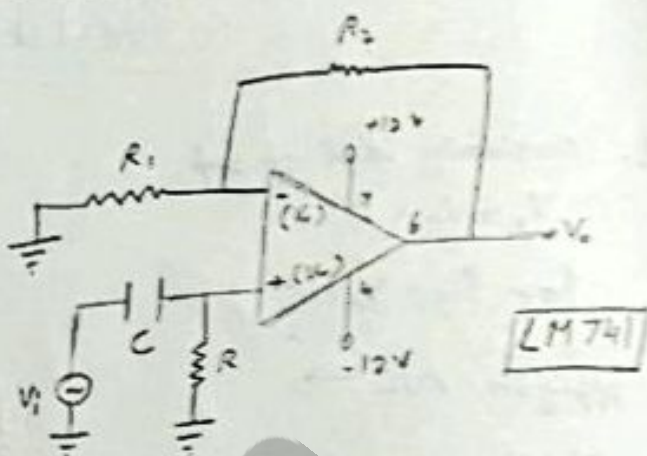∴ Theoretical value of
cut-off frequency = 1.59 kHz



By
21.05.22

PART-A :

Inverting Amplifier :

1. $R_1 = 10\text{K}\Omega$ and $R_2 = 1\text{K}\Omega$

2. from function generator

$V_i \Rightarrow V_{pp} = 200\text{mV}$ frequency = 1KHz

3. voltage gain $\rightarrow A = \frac{V_o}{V_i}$

$V_i (\text{mV})$	$V_o (\text{mV})$	$A = \frac{V_o}{V_i}$
200	-2100	-10.5
100	-1000	-10
280	-2700	-9.6

phase difference between V_o and $V_i = 180^\circ$ (out of phase)

so gain $\Rightarrow -ve$


4. change $R_1 = 100\text{K}\Omega$ and $R_2 = 10\text{K}\Omega$

$V_i (\text{mV})$	$V_o (\text{mV})$	$A = \frac{V_o}{V_i}$
104	-1040	-10
200	-2000	-10
280	-2800	-10

5 & 6:

Keeping V_i at 200mV_{pp}

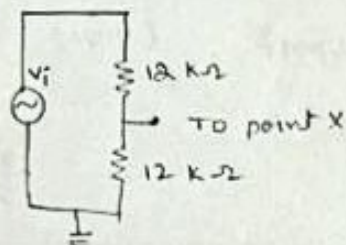
first we make potential divider - in circuit



Then $\frac{V_o}{V_i}$ is

- (i) $R_1 = 100\text{k}\Omega$ and $R_2 = 10\text{k}\Omega$
 (ii) $R_1 = 10\text{k}\Omega$ and $R_2 = 1\text{k}\Omega$

Resistances	V_i (mv)	V_o (mv)	$A = \frac{V_o}{V_i}$
$R_1 = 100\text{k}\Omega$ $R_2 = 10\text{k}\Omega$	200	-620	-3.1
$R_1 = 10\text{k}\Omega$ $R_2 = 1\text{k}\Omega$	200	-140	-0.7

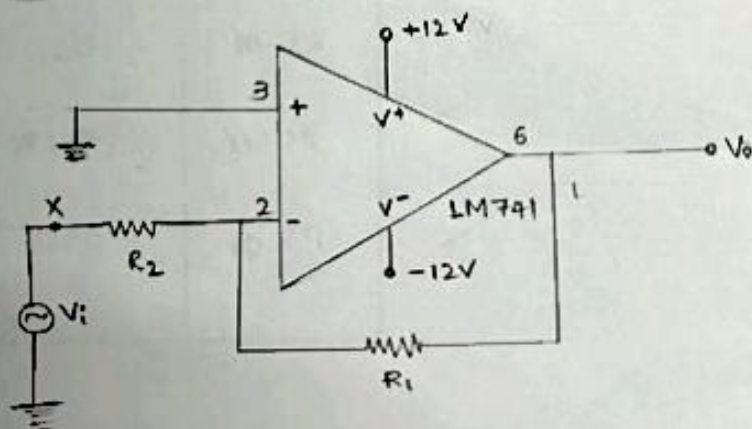

For inverting Amplifier

PART - B :

Non-inverting Amplifier

1. $R_1 = 10 \text{ k}\Omega$ and $R_2 = 1 \text{ k}\Omega$
2. $V_i = 200 \text{ mV}$ (V_{p-p}) , frequency = 1 kHz
3. Gain $A = \frac{V_o}{V_i}$

V_i (mV)	V_o (mV)	$A = \frac{V_o}{V_i}$
200	2200	11
108	1160	10.74
290	3200	11.03

phase difference between V_o and $V_i = 0^\circ$
 same phase
 so, gain $\Rightarrow$ +ve


4. change $R_1 = 100 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$

V_i (mV)	V_o (mV)	$A = \frac{V_o}{V_i}$
102	1100	10.78
190	2100	11.05
290	3100	10.69

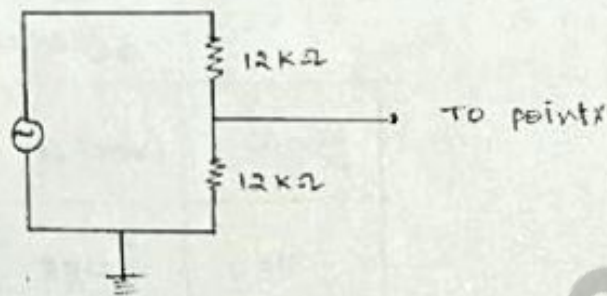546.

$$V_i = 200 \text{ mV (vp-p)}$$


first we make potential divider in circuit



Then we compute $\frac{V_o}{V_i}$

- i) $R_1 = 100 \text{ k}\Omega$ & $R_2 = 10 \text{ k}\Omega$
- ii) $R_1 = 10 \text{ k}\Omega$ & $R_2 = 1 \text{ k}\Omega$


Resistances	V_i (mV)	V_o (mV)	$A = \frac{V_o}{V_i}$
$R_1 = 100 \text{ k}\Omega$ $R_2 = 10 \text{ k}\Omega$	200	1100	5.5
$R_1 = 10 \text{ k}\Omega$ $R_2 = 1 \text{ k}\Omega$	200	1080	5.4

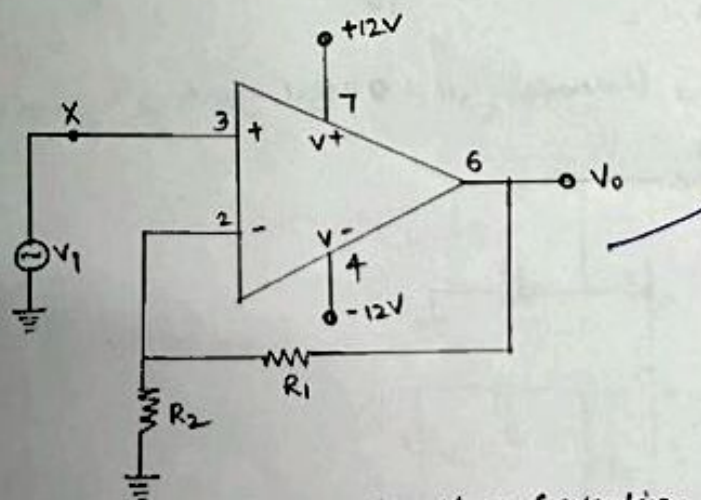

for Non-inverting Amplifier

Input
 $f_{cut-off} = 1.8 \text{ kHz}$
 Output gain = 1.0

(Gain) A_v

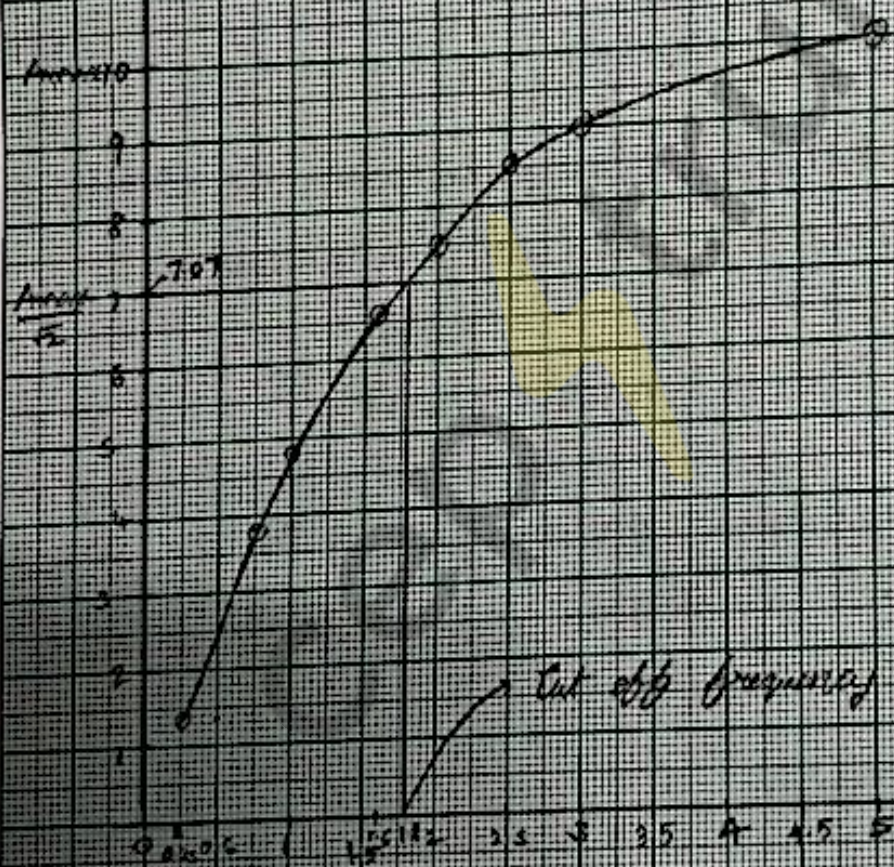

For Non-inverting high pass filter

Date
 21/5/22

PART-D :

1. For a source with high internal impedance, a non-inverting op-amp will be suitable.

Reason: for an inverting amplifier:

$$A = -\frac{R_f}{R_i(I)}$$

Here, $A = \text{gain}$;

R_f = output impedance

R_i = Input impedance

for a non-inverting amplifier: $A = 1 + \frac{R_f}{R_i(NI)}$

Now, in comparing the magnitude of gain,
by keeping A & R_f same in both cases,

we see

$$R_i(NI) > R_i(I)$$

So, we need non-inverting amplifier, for
high internal impedance

Basanta
29/5/22.