

Testbench in VERILOG


Dr. Chandan Karfa

Department of Computer Science and Engineering



 भारतीय प्रौद्योगिकी संस्थान गुवाहाटी
INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI






Testbench

**Test vector generator
and
Monitor**

**Design Under Test
(DUT)**

 

Connection by Position

```
module child_mod (sig_a, sig_b,  
sig_c, sig_d);  
  input    sig_a, sig_b;  
  output   sig_c, sig_d;
```


```
  // module description goes here.
```

```
endmodule
```

```
module parent_mod;  
  wire [4:0] g;  
  
  child_mod G1 (g[3], g[1], g[0], g[2]);
```

```
  // Listed order is significant  
endmodule
```

parent_mod

 


Connection by Name

```
module child_mod (sig_a, sig_b,  
sig_c, sig_d);  
  input    sig_a, sig_b;  
  output   sig_c, sig_d;  
  
  // module description goes here.  
  
endmodule
```

```
module parent_mod;  
  wire [3:0] g;  
  //order is not significant  
  child_mod G1 ( .sig_c(g[0]),  
                .sig_a(g[3]),  
                .sig_d(g[2]),  
                .sig_b(g[1]));  
  
endmodule
```

parent_mod

 

Recommended style!

Delay

Time duration between assignment from RHS to LHS.

- Inter assignment delay (**Delayed execution**)

`#10 q = x + y ;`

It simply waits for the appropriate number of time steps before executing the command.

- Intra assignment delay (**Delayed assignment**)

`q = #10 x + y ;`

Value of $x + y$ is calculated at the time that the assignment is executed, but this value is not assigned to q until after the delay period, regardless of whether or not x or y have changed during that time.

Inter-assignment	<code>#5 a = b ;</code>	<code>#5 ; a = b ;</code>
Intra-assignment	<code>a = #5 b ;</code>	<code>temp = b ; #5 ; a = temp ;</code>

```

module testbench ;
  wire w1, w2, w3 ;
  DUT U1 (w1, w2, w3) ;
  Test T1 (w1, w2, w3) ;
endmodule

```

```


module DUT (out, in_1, in_2) ;
  output out ;
  input in_1, in_2 ;
  assign out = in_1 & in_2 ;
endmodule

```

```

module Test (out, in_1, in_2) ;
  input out ;
  output reg in_1, in_2 ;
  initial
  begin
    $monitor ($time, "in_1 = %b, in_2 = %b, out = %b", in_1, in_2, out) ;
    in_1 = 0 ; in_2 = 0 ;
    #10 in_1 = 0 ; in_2 = 1 ;
    #10 in_1 = 1 ; in_2 = 0 ;
    #10 in_1 = 1 ; in_2 = 1 ;
    #10 $finish ;
  end
endmodule

```

 

Output Log:

```

0: in_1 = 0, in_2 = 0, out = 0
10: in_1 = 0, in_2 = 1, out = 0
20: in_1 = 1, in_2 = 0, out = 0
30: in_1 = 1, in_2 = 1, out = 1

```

Compiler Directives and System Tasks

- **`define**: used to define a text macro.
- **`include**: used to include content of some other file inside a verilog code.
- **\$time**: It returns the current simulation time as 64-bit integer value. However this value will be scaled to the `timescale unit.
- **\$monitor**: It continuously monitors the changes in any one of the variable specified in the parameter list. Whenever, anyone of them changes, it displays the formatted string specified within double quotes.
- **\$finish** : It terminates the simulation.

Compiler Directives and System Tasks

`timescale <ref_time_unit>/<precision>

Example: `timescale 1ns/ 100 ps

Time values to be read as **ns** and to be rounded to the nearest 100 **ps**.

`timescale 10ns / 10ns

#1.5 ;

1.5 x 10 ns = 15 ns.

Rounded to 20 ns.

`timescale 1ns / 1ps

#1 ; // 1 ns delay

#0.001; // 1 ps. This is the minimum delay you can have with this time scale.

#0.0001; // this will give 0 ns delay.

Testbench

**Clock generation
block**


clk

clk

clk

**Test vector generator
and
Monitor**

**Design Under Test
(DUT)**

 

Clock generation with 50% duty cycle

```
initial clk = 0 ;  
always #10 clk = ~clk ;
```


```
always  
begin  
    clk = 0 ;  
    #10 ;  
    clk = 1 ;  
    #10 ;  
end
```

```
parameter CLOCK_PERIOD = 5  
always # (CLOCK_PERIOD / 2) clk = ~clk ;
```

Clock generation with variable duty cycle

```
module clk_gen (output clk) ;  
    parameter CLK_PERIOD = 10;  
    parameter DUTY_CYCLE = 60; //60% duty cycle  
    parameter TCLK_HI = (CLK_PERIOD*DUTY_CYCLE/100);  
    parameter TCLK_LO = (CLK_PERIOD-TCLK_HI);  
  
    reg clk;  
  
    initial  
        clk = 0;  
  
    always  
    begin  
        #TCLK_LO;  
        clk = 1'b1;  
        #TCLK_HI;  
        clk = 1'b0;  
    end  
endmodule
```

Example: Synchronous FIFO

 

```
module FIFO # (parameter DATA_WIDTH = 8,  
               parameter FIFO_DEPTH = 10)  
    (Data_out, Full, Empty, Data_In, Wr_En_  
     Rd_En, clk, reset) ;
```



```
module FIFO # (parameter DATA_WIDTH = 8,  
               parameter FIFO_DEPTH = 32)  
  (Data_out, Full, Empty, Data_In, wr_en, rd_en, clk, reset) ;  
  
  input [DATA_WIDTH - 1 : 0] Data_In ;  
  input wr_en ;  
  input rd_en ;  
  input clk ;  
  input reset ;  
  
  output reg [DATA_WIDTH - 1 : 0] Data_Out ;  
  output reg Full ;  
  output reg Empty ;  
  
  reg [DATA_WIDTH - 1 : 0] memory [FIFO_DEPTH - 1 : 0] ;  
  reg [FIFO_DEPTH - 1 : 0] rd_ptr, wr_ptr, depth_cnt ;
```

```
//PUSH
always @ (posedge clk)
begin
    if (reset) begin
        wr_ptr <= 'h0 ;
    end
    else begin
        if (wr_en && !Full) begin
            memory [wr_ptr] <= Data_In ;
            wr_ptr <= wr_ptr + 1 ;
        end
    end
end
end
```




```
//POP
always @ (posedge clk)
begin
    if (reset) begin
        rd_ptr <= 'h0 ;
    end
    else begin
        if (rd_en && !Empty) begin
            Data_out <= memory [rd_ptr] ;
            rd_ptr <= rd_ptr + 1 ;
        end
    end
end
end
```

```


//Depth Count
always @ (posedge clk)
begin
    if (reset) begin
        depth_cnt <= 'h0 ;
    end
    else begin
        if (wr_en && !Full)
            depth_cnt <= depth_cnt + 1 ;
        else if (rd_en && !Empty)
            depth_cnt <= depth_cnt - 1 ;
        //add one more condition to check simultaneous WR & RD.
    end
end

assign Empty = (depth_cnt == 'h0)? 1 : 0 ;
assign Full   = (depth_cnt == FIFO_DEPTH)? 1 : 0 ;
endmodule

```

 

```
module testbench # (parameter DATA_WIDTH = 8,  
                    parameter FIFO_DEPTH = 8);  
    wire clk, reset ;  
    wire rd_en, wr_en, Full, Empty ;  
    wire [DATA_WIDTH - 1 : 0] data_tf, data_ft;  
  
    FIFO ff(.clk (clk), .reset (reset),  
           .Full (Full), .Empty (Empty),  
           .wr_en (wr_en), .rd_en(rd_en),  
           .Data_In (data_tf), .Data_out (data_ft)) ;  
  
    Test_FIFO tt(.Data_out (data_tf), .Full (Full),  
                .Empty (Empty), .Data_in(data_ft),  
                .wr_en(wr_en), .rd_en(rd_en),  
                .clk (clk), .reset(reset)) ;  
  
    clk_gen cg(.clk (clk)) ;  
  
endmodule
```

 

From Instance and Process Name, select “design Top”. Then from “Objects”, select required objects and the right click to “add to wavewindow”.

Verilog Coding Guidelines

- When modeling sequential logic, use non-blocking assignments.
- When modeling latches, use non-blocking assignments.
- When modeling combinational logic with an always block, use blocking assignments.
- When modeling both sequential and combinational logic within the same always block, use non-blocking assignments.
- Do not mix blocking and non-blocking assignments in the same always block.
- Do not make assignments to the same variable from more than one always block.

Thank You